

Second Edition

Analog circuit Drill

S**olutions**
Test Drill I
Test Drill II

A K Tripathi
MD, Mechasoft Publishers and Educators
and
Asstt. Prof. Electronics Engineering Department
IERT, Degree Division, Allahabad (INDIA)

 Mechasoft Publishers, Allahabad (INDIA)

Solutions


Analog circuit Drill

Test Drill I

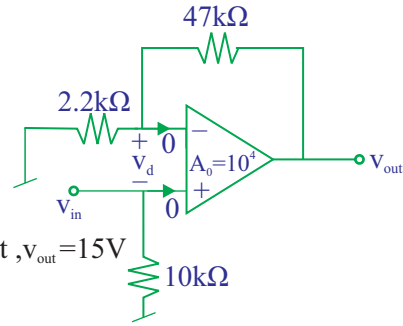Q1. Assume linear operation to get

$$v_{out} = v_{in} \times \frac{1 + \frac{47}{2.2}}{1 + \frac{47}{10^4}} = 1 \times \frac{22.36}{1 + 22.36 \times 10^{-4}} = 22.31V$$


Since, calculation gives $v_{out} > 15V$, op-amp is in saturation. In fact, $v_{out} = 15V$ and $v_d = 15 \times 10^{-4} V = 1.5mV$



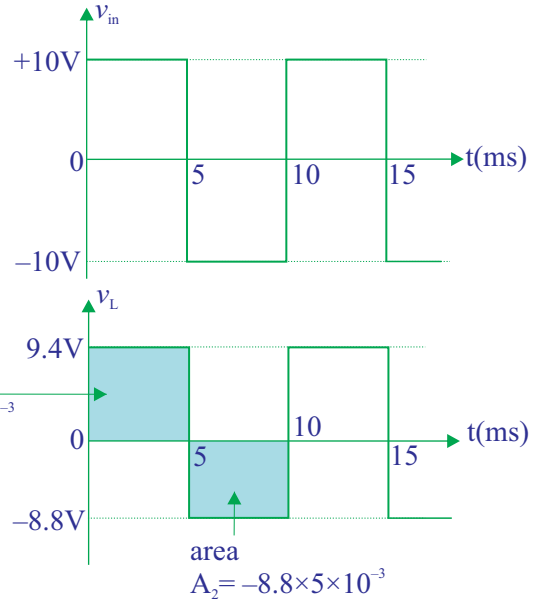Q2. $f = 100Hz$

$$T = \frac{1}{100} = 0.01 = 10msec$$


$$dc \text{ component} = \frac{\text{area over one time period}}{T} = \frac{A_1 + A_2}{T} = \frac{9.4 \times 5 \times 10^{-3} - 8.8 \times 5 \times 10^{-3}}{10 \times 10^{-3}} = 0.3V$$



Q3. Let $v_{in} = A \sin \omega_0 t$. Then, $v_{out} = -\left(10 \times 10^3 \times 0.01 \times 10^{-6}\right) \frac{d}{dt} (A \sin \omega_0 t)$
 $= -10^{-4} A \omega_0 \cos \omega_0 t$


$|v_{in}| = |v_{out}| \Rightarrow A = 10^{-4} A \omega_0 \Rightarrow \omega_0 = 10 \text{krad/sec}$ and $f_0 = \frac{10}{2\pi} = 1.59 \text{kHz}$

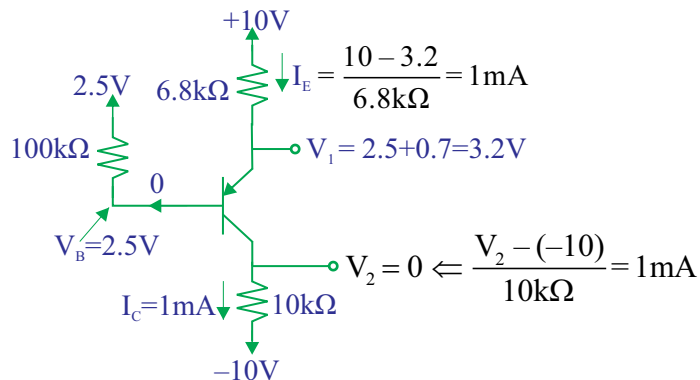Q4. (c) $V_1 - V_2 = 3.2V$ as demonstrated below.




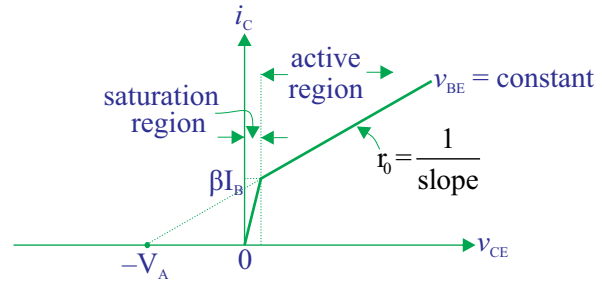Q5. The output resistance

$$r_0 = \frac{V_A}{\beta I_B} = \frac{200}{100 \times 50 \times 10^{-6}} = 4 \times 10^4 \Omega = 40k\Omega$$



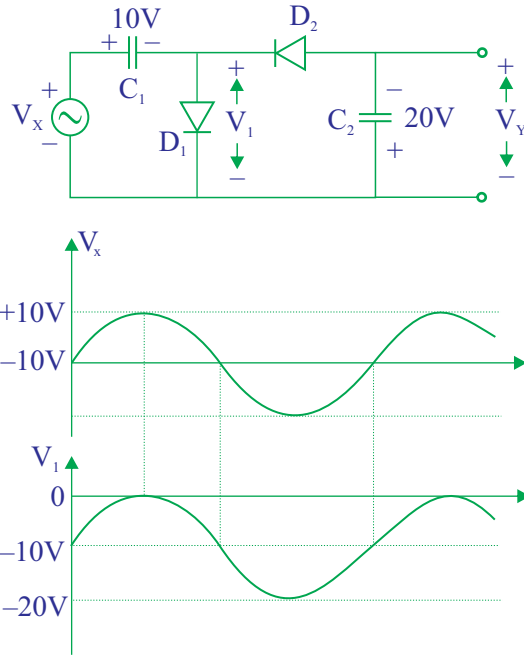
Q6. (c) When V_x varies sinusoidally from zero to peak value 10V, the capacitor C_1 charges instantaneously to 10V with polarity as shown, while D_1 remains on. After C_1 has charged to 10V, D_1 turns off and in steady state, $V_1 = V_x - 10 = 10\cos\omega t - 10$ has extremities at 0 and $-20V$ as depicted below. While V_1 varies from 0 to $-20V$, D_2 turns on to allow the capacitor C_2 to charge instantaneously to 20V with polarity as shown. Thereafter, D_2 turns off and C_2 does not find any path to discharge. Thus, $V_Y = -20V$.



Q7.(d) $\alpha = 1 \Rightarrow I_B = 0$ and $I_C = I_E = 1\text{mA}$

$$\frac{-4 - (-10)}{R_C} = \frac{10 - 0.7}{R_E} = 1\text{mA}$$

$R_E = 9.3k\Omega$ and $R_C = 6k\Omega$

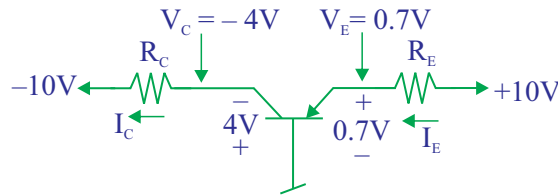

Q8(b). Q_1 and Q_2 both are in saturation.

$$K(V_{GS1} - V_t)^2 = K(V_{GS2} - V_t)^2; V_{GS1} = V_{DD} - V_B \text{ and } V_{GS2} = V_A$$

$$(V_{DD} - V_B - V_t)^2 = (V_A - V_t)^2$$

$$V_{DD} - V_B - V_t = \pm (V_A - V_t)$$

either $V_{DD} - V_B - V_t = V_A - V_t \Rightarrow V_{DD} = V_A + V_B$

or $V_{DD} - V_B - V_t = V_t - V_A$

but $V_{GS1} = V_{DD} - V_B$ must be greater than V_t , that is, $V_{DD} - V_B - V_t$ must be positive and this demands $V_t > V_A$ which is not possible. In fact, $V_{GS2} = V_A$ must be greater than V_t . Thus, $V_{DD} = V_A + V_B$

Q9. The diodes D_1 and D_3 turn on when $v_{in} > 1.2V$ while the diodes D_2 and D_4 turn on when $v_{in} < -1.2V$.

During time $t \in [25ms, 100ms]$, when V_{in} decreases from $+1.2V$ to $-1.2V$, all diodes D_1, D_2, D_3 and D_4 remain off and $i_L = 0$.


The equation of line segment AB is

$$y - 5 = \frac{-10 - 5}{100 - 25} (x - 25) \quad ; \quad y \text{ represents } v_{in} \text{ and } x \text{ represents time } t, \text{ in ms}$$

$$v_{in} = -0.2t + 10$$

$$1.2 = -0.2t_1 + 10 \text{ gives } t_1 = 44\text{ms} \text{ and } -1.2 = -0.2t_2 + 10 \text{ gives } t_2 = 56\text{ms}$$
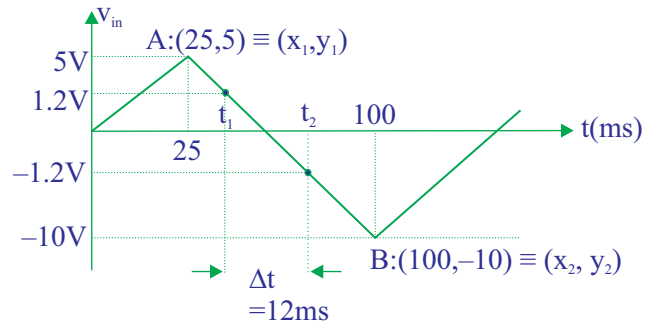
$$\Delta t = t_2 - t_1 = 56 - 44 = 12\text{ms}$$




Q10. $I_{ios} = 0 \Rightarrow I_{B1} - I_{B2} = 0 \Rightarrow I_{B1} = I_{B2}$

$$V = -I_{B2} R_X \text{ and } I_1 = \frac{0 - V}{R_1} = \frac{I_{B2} R_X}{R_1}$$

$$I_2 = I_1 - I_{B1} = \frac{I_{B2} R_X}{R_1} - I_{B1}$$

$$V - I_2 R_2 = V_2 = 0 \Rightarrow -I_{B2} R_X - \left[\frac{I_{B2} R_X}{R_1} - I_{B1} \right] R_2 = 0 \quad ; \quad I_{B1} = I_{B2}$$
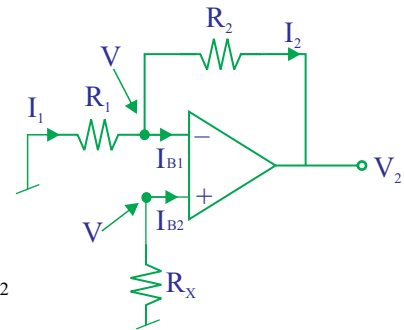
$$R_X + \frac{R_X R_2}{R_1} = R_2 \Rightarrow R_X = \frac{R_1 R_2}{R_1 + R_2} = \frac{5 \times 7.5}{5 + 7.5} = 3\text{k}\Omega$$




Q11(a). For $v_i > 0$, diode D is reverse biased and $v_2 = v_i$.

For $v_i < 0$, diode D is forward biased and $v_2 = -v_i$.

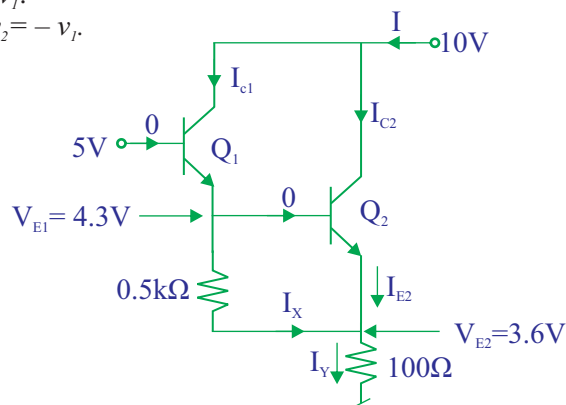Q12(b). $V_{E2} = 5 - 0.7 - 0.7 = 3.6V$

$$I_Y = \frac{3.6}{100} \text{ A} = 36\text{mA}$$

$$I = I_{C1} + I_{C2} = I_X + I_{E2} = I_Y = 36\text{mA}$$



Q13(c). For PLL in lock mode

$$\omega_i = \omega_0 + k_v \times V_C$$

$$\text{and } V_C = \frac{\omega_i - \omega_0}{k_v} = \frac{2\pi(f_i - f_0)}{2\pi \times 10^3} = \frac{250 - 500}{10^3} = -0.25V$$


Q14. The circuit for $b_1 b_2 b_3 = 011$, is sketched below.

$$I_0 = I_1 + I_2$$

$$\frac{0 - v_0}{R} = \frac{5 - 0}{4R} + \frac{5 - 0}{8R}$$

$$v_0 = -(1.25 + 0.625)$$


$$= -1.875V$$

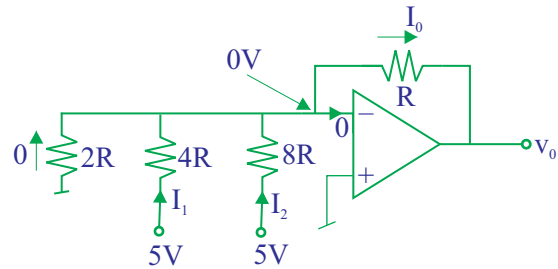

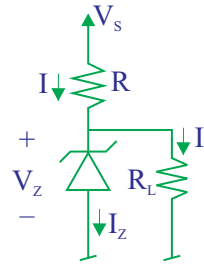Q15(b). $I_Z = I - I_L > 0$ or $I > I_L$ ensures consistent regulation.

$$\frac{V_s - V_Z}{R} > \frac{V_Z}{R_L}$$

$$R_L > R \left[\frac{V_Z}{V_s - V_Z} \right] \text{ or } R_L > R \left[\frac{V_s}{V_Z} - 1 \right]^{-1}$$



Q16. The diode ac resistance, $r_f = \frac{V_T}{I} = \frac{25mV}{0.1mA} = 250\Omega$

$$v_y = \frac{v_x r_f}{r_f + r_x} = \frac{250 v_x}{250 + 250} = \frac{v_x}{2}$$

$$v_y = 0.5 v_x \Rightarrow \lambda = 0.5$$


Q17(b). $v_0(t) = \left[\lambda \cos(10^4 t) \right] \left(1 + \frac{90}{10} \right) = 10\lambda \cos 10^4 t \text{ V}$

$$\dot{v}_0(t) = 10^5 \lambda \cos 10^4 t \text{ and } \dot{v}_0(t)_{\max} = 10^5 \lambda \text{ V/sec}$$

$$\text{For no distortion, } \dot{v}_0(t)_{\max} \leq 0.4 \times 10^6 \Rightarrow 10^5 \lambda \leq 0.4 \times 10^6$$

$$\lambda \leq 4V$$

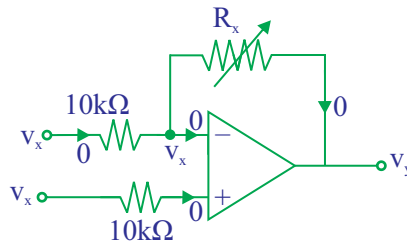
Q18(b). $v_y = v_x$
The current through R_x is zero.



Q19(b). $I_1 = I_2 = \frac{0.25 - 0}{1k\Omega} = 0.25mA$ and $\frac{0 - V_0}{10k\Omega} = 0.25mA \Rightarrow V_0 = -2.5V$

$$I_2 + I_L = I \leq 25mA \Rightarrow \left[0.25mA + \frac{2.5}{R_L} \right] \leq 25mA$$


$$R_L \geq 100\Omega$$

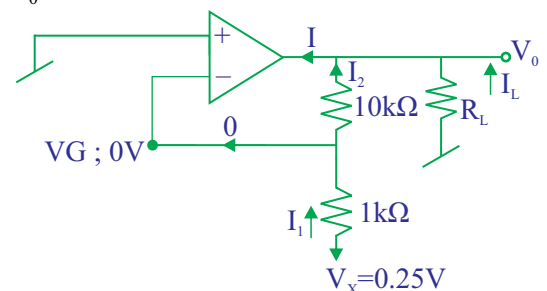

Q20. The gain-band width product,
 $GBP = A_0 f_p = (100\text{dB}) \times 4\text{Hz} = (10^5 \text{V/V}) \times 4\text{Hz} = 400\text{kHz}$

$$|A_{fb}| = 100 \text{ and band width } f_b = \frac{A_0 f_p}{|A_{fb}|} = \frac{400\text{kHz}}{100} = 4\text{kHz}$$

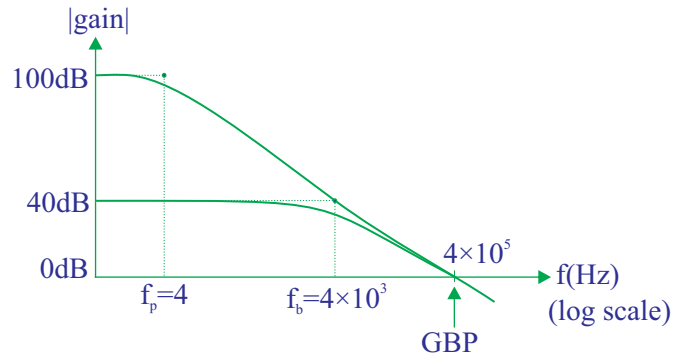It is important to note that GBP remains constant .



Q21(a) The dc equivalent circuit is sketched below with ac source v_s shorted. Transistors Q_a , Q_b and Q_c are in saturation, have equal drain currents and equal $V_{GS} = 5V$.

Assume Q_3 in saturation.

$$I_{D3} = K_3 (V_{GS3} - V_t)^2 = [8\text{mA}/V^2] (5-3-1)^2 = 8\text{mA}$$

Q_1 and Q_2 are identical and allow equal drain currents.

$$\text{Let } V_{GS1} = V_{GS2} = V_1$$

$$I_{D1} = I_{D3} \Rightarrow K_1 (V_{GS1} - V_t)^2 = 8\text{mA} \Rightarrow (V_1 - 1)^2 = 8$$


$$V_1 = 1 \pm 2\sqrt{2} \text{ V}$$

Since, V_1 can not be negative, $V_1 = 1 + 2\sqrt{2} = 3.83\text{V}$

$$V_{OUT} = 15 - 2 \times 3.83 = 7.34\text{V}$$

Note that $V_{GD3} = 5 - 7.34 = -2.34 < V_t$; $V_t = 1\text{V}$,

Q_3 is, indeed, in saturation.

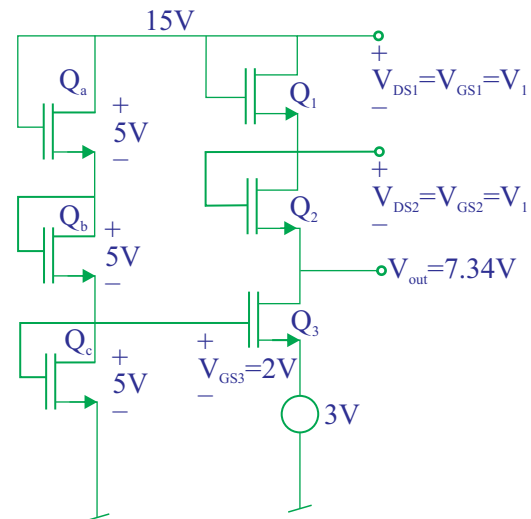

Q22(a). $I_{D1} = I_{ref} = \frac{1}{2} K'_n (V_{GS1} - V_t)^2$


$$100 \times 10^{-6} = \frac{1}{2} \times 200 \times 10^{-6} (V_{GS1} - 1)^2 \Rightarrow V_{GS1} = 1 \pm 1 = 0 \text{ or } 2\text{V}$$

Note that V_{GS} can not be 0. So, $V_{GS1} = 2\text{V}$ and $R_x = \frac{5-2}{100\mu\text{A}} = 30\text{k}\Omega$

The transistor Q_2 will remain in saturation if $V_{DS} \geq V_{GS} - V_t$ or $V_o \geq 2 - 1$ or $V_o \geq 1\text{V}$.

$$V_{o, \min} = 1\text{V}$$

Q23(b).

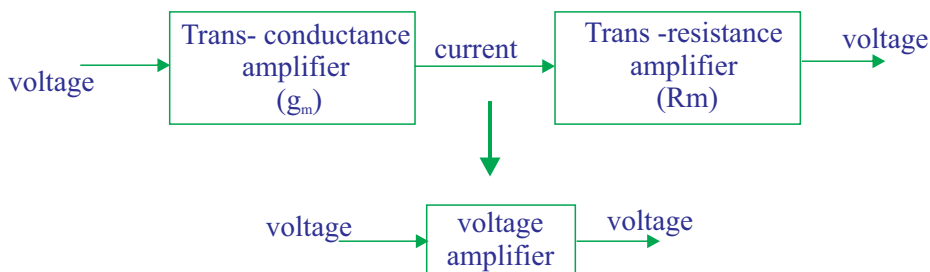

Q24(d). Corrigendum; please note that Fig.(b) shows relation between v_x and v_y , and not between v_x and v_z .
The error in Q24 is regretted.

$$v_y = -v_x \text{ for } v_x > 0 \\ = 0 \text{ for } v_x < 0$$

$$v_z = -v_x - 2v_y = -v_x - 2(-v_x) = v_x \text{ for } v_x > 0 \\ = -(-v_x) - 2 \times 0 = v_x \text{ for } v_x < 0$$

The block diagram realizes absolute value operation .

Q25(b). $g_m = \frac{I_{CQ}}{V_T} \Rightarrow \frac{0.8 \text{ mA}}{26 \text{ mV}} \leq g_m \leq \frac{1.2 \text{ mA}}{26 \text{ mV}}$ or $30.77 \leq g_m \leq 46.15 \text{ mA/V}$

$$r_{\pi, \max} = \frac{\beta_{\max}}{g_{m, \min}} = \frac{180}{30.77 \times 10^{-3}} = 5.85 \text{ k}\Omega$$



Analog circuit Drill

Test Drill II

Q1(c). **Corrigendum** : the value of v_- at $t = 100ms$ is to be evaluated.

At $t = 0$, $v_{out} = 0$ and $v_C = 0$.

In linear region for $t > 0$

$$v_{out} = -\frac{1}{20 \times 10^3 \times 1 \times 10^{-6}} \int_0^t v_{in}(t) dt = -50 \int_0^t 2 dt = -100t \text{ while } v_C(t) = 0 - v_{out} = 100t.$$

The output voltage v_{out} will linearly fall and reach saturation limit of $-8V$ at time

$$t_1 = \frac{-8}{-100} = 0.08 \text{sec} = 80 \text{ms} \text{ while } v_C|_{t=80 \text{ms}} = 8V$$



For $t > t_1$ or $t > 80ms$, the op amp is no more in linear region and inverting terminal of op amp is no more at virtual ground. The capacitor charges exponentially with time constant $\tau = 20 \times 10^3 \times 10^{-6} = 20 \times 10^{-3} = 20ms$ till the voltage at inverting terminal $v_- = 2V$ and $v_C = v_- - v_{out} = 2 - (-8) = 10V$.

$$\text{For } t > t_1, v_C(t) = v_C(t_1) + [v_C(\infty) - v_C(t_1)](1 - e^{-(t-t_1)/\tau}) = 8 + (10 - 8)(1 - e^{-(t-t_1)/\tau}) = 8 + 2(1 - e^{-(t-t_1)/\tau})$$

$$\text{and } v_- = v_{out} + v_C = -8 + 8 + 2(1 - e^{-(t-t_1)/\tau}) = 2(1 - e^{-(t-t_1)/\tau})$$

$$v_C(t)|_{t=100 \text{ms}} = 8 + 2[1 - e^{-(100-80)/20}] = 9.26V$$

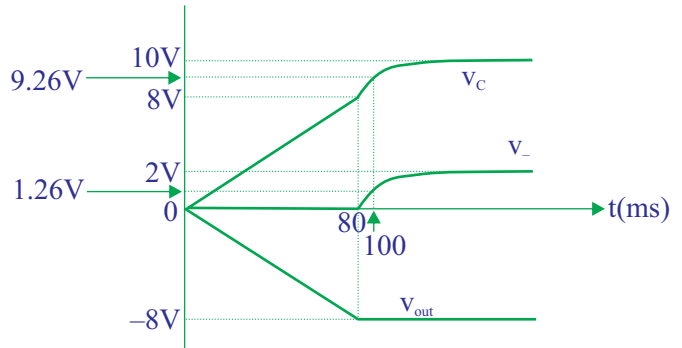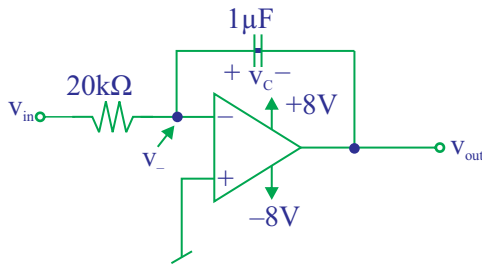
$$\text{At } t = 100ms, v_C = 9.26V, v_{out} = -8V \text{ and } v_- = v_{out} + v_C = -8 + 9.26 = 1.26V$$



$$I_{B_1} = I_{B_2} = 0 \text{ and } I_{C_1} = \frac{5.4 - 0.7}{4.7k\Omega} = 1 \text{mA}$$

$$\text{Q2. } I_{C_2} = 2 I_{C_1} = 2 \text{mA} = I_{C_3} \text{ and } g_{m_3} = \frac{I_{C_3}}{V_T} = \frac{2 \text{mA}}{25 \text{mA}} = 0.08 \text{ A/V}$$
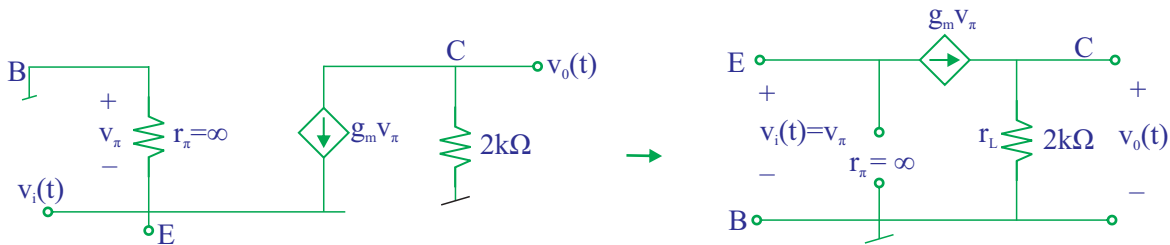
$$\text{Q}_3 \text{ has } g_m = 0.08 \text{ A/V and } r_\pi = \frac{\beta}{g_m} = \infty$$



$$v_o(t) = g_m v_\pi r_L = g_m v_i(t) r_L = 0.08 \times 10^{-2} \cos(1000\pi t) \times 2 \times 10^3 \Rightarrow V_o = 1.6V$$

Q3. Both transistors M_1 and M_2 have $V_{GD} = 0$ and therefore, both M_1 and M_2 are obviously in saturation .

$$I = 0.5I_1 \Rightarrow I_1 = I_2$$

$$K_1(V_{GS1} - V_{t1})^2 = K_2(V_{GS2} - V_{t2})^2 ; V_{GS1} = V_{GS2} = V_x$$

$$K_1(V_x - V_{t1})^2 = K_2(V_x - V_{t2})^2$$

$$0.5 \times 10^{-3}(V_x - 1)^2 = 2 \times 10^{-3}(V_x - 2)^2 \text{ or } V_x - 1 = \pm 2(V_x - 2)$$

$$V_x - 1 = 2(V_x - 2) \text{ gives } V_x = 3V \text{ and } V_x - 1 = -2(V_x - 2) \text{ gives } V_x = \frac{5}{3} V$$

Note that $V_{GS1} = V_{GS2} = V_x$ must be larger than V_{t1} and V_{t2} both . Thus, $V_x = 3V$

Q4. The circuit is re-sketched below in more convenient form .

$$\frac{1 - V_1}{R} = \frac{V_1}{R} + \frac{V_1 - V}{R} \text{ gives } V_1 = \frac{1 + V}{3}$$

$$\frac{V_1 - V}{R} = \frac{V}{R} \text{ gives } V = \frac{V_1}{2} = \frac{1}{2} \left[\frac{1 + V}{3} \right] \Rightarrow V = 0.2$$


$$\frac{1 - V_2}{R + \Delta R} = \frac{V_2}{R} + \frac{V_2 - V}{R} \text{ and } \frac{V_2 - V}{R} = \frac{V - V_y}{R}$$

$$\frac{1 - V_2}{R + \Delta R} = \frac{V_2}{R} + \frac{V_2 - 0.2}{R} \text{ and } V_2 - 0.2 = 0.2 - V_y \Rightarrow V_2 = 0.4 - V_y$$

$$\frac{1 - (0.4 - V_y)}{R + \Delta R} = \frac{0.4 - V_y}{R} + \frac{0.4 - V_y - 0.2}{R}$$



$$\frac{0.6 + V_y}{1 + \frac{\Delta R}{R}} = 0.4 + 0.4 - 0.2 - 2V_y ; \frac{\Delta R}{R} = 0.06$$
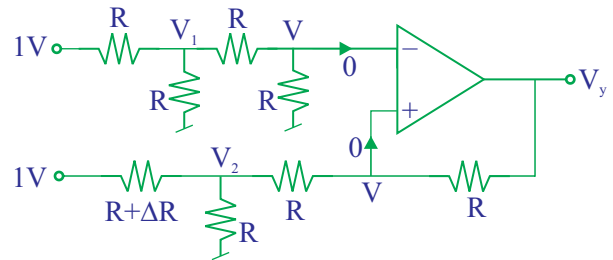
$$\frac{0.6 + V_y}{1 + 0.06} = 0.6 - 2V_y \Rightarrow V_y = 0.011538V = 11.54mV$$



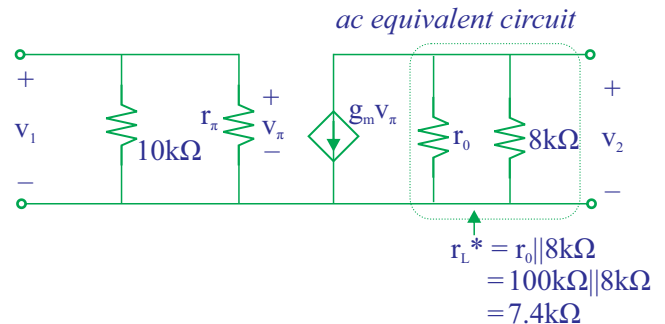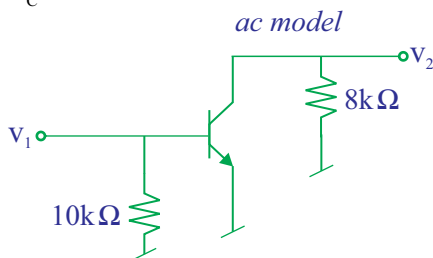Q5(c). $g_m = \frac{I_C}{V_T} = \frac{1mA}{25mV} = 0.04 \text{ A/V}, r_\pi = \frac{\beta}{g_m} = \frac{100}{0.04} = 2500\Omega = 2.5k\Omega$

$$r_o = \frac{V_A}{I_C} = \frac{100V}{1mA} = 100k\Omega$$



$$v_2 = -g_m v_\pi r_L^* ; v_\pi = v_1$$

$$\frac{v_2}{v_1} = -0.04 \times 7.4 \times 10^3 = -296 \text{ and } \left| \frac{v_2}{v_1} \right| = 296$$

Q6. $I_C = I_S e^{V_{BE}/V_T}$ and $V_{BE} = V_T \ln(I_C / I_S)$


$$V_{BE1} = V_{BE2} + I_{C2} R_2$$

$$V_T \ln\left(\frac{I_{C1}}{I_S}\right) = V_T \ln\left(\frac{I_{C2}}{I_S}\right) + 5 \times 10^{-6} R_2$$

$$I_{C1} = \frac{5 - 0.7}{4.3k\Omega} = 1mA$$

$$V_T \ln\left(\frac{I_{C1}}{I_{C2}}\right) = 5 \times 10^{-6} R_2 \Rightarrow 25 \times 10^{-3} \ln\left(\frac{10^{-3}}{5 \times 10^{-6}}\right) = 5 \times 10^{-6} R_2$$
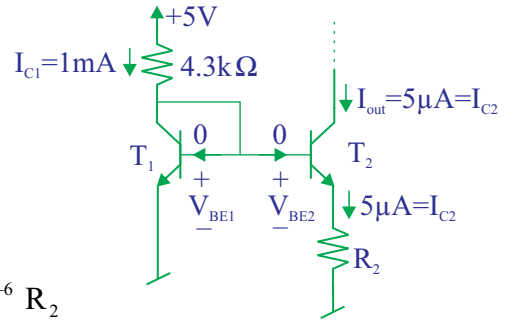
$$R_2 = 0.02649 \times 10^6 \Omega = 26.5k\Omega$$



Q7. Assuming saturation

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$= \frac{1}{2} \times 100 \times 10^{-6} \times 50 (1 - 0.8)^2$$

$$= 100 \times 10^{-6} A = 100\mu A$$


$$V_D = 5 - 100 \times 10^{-6} \times 5 \times 10^3 = 4.5V$$

$$V_{GD} = 1 - 4.5 = -3.5V$$



Since, $V_{GD} < V_t$, the saturation mode of operation is justified.

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t) = 100 \times 10^{-6} \times 50 (1 - 0.8) = 10^{-3} A/V$$

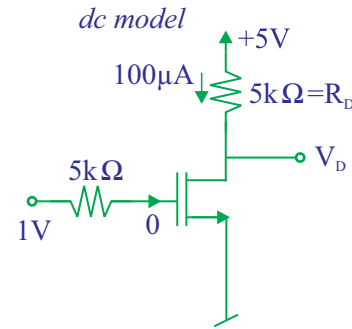For $\lambda = 0$, $V_A = \infty$ and $r_o = \infty$



ac model

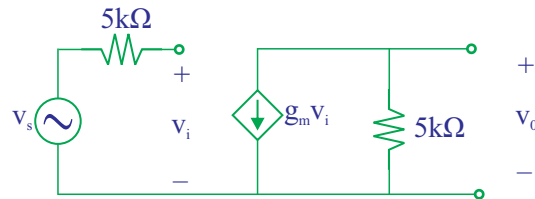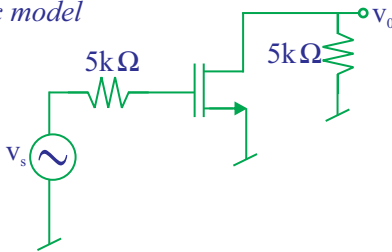


$$v_0 = -g_m v_i \times 5 \times 10^3 ; v_i = v_s$$

$$\left| \frac{v_0}{v_s} \right| = 10^{-3} \times 5 \times 10^3 = 5$$

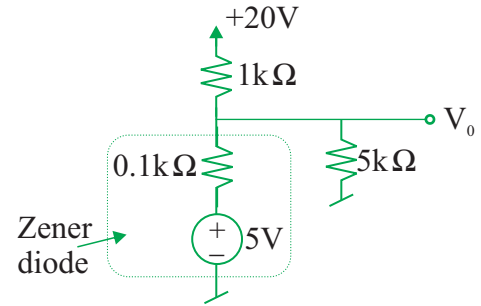Q8(c). $\frac{V_0 - 20}{1k\Omega} + \frac{V_0 - 0}{5k\Omega} + \frac{V_0 - 5}{0.1k\Omega} = 0$
 $5V_0 - 100 + V_0 + 50V_0 - 250 = 0$
 $V_D = 6.25V$


$P_Z = I_Z^2 R_Z + V_Z I_Z ; I_Z = \frac{6.25 - 5}{0.1k\Omega} = 12.5mA$
 $= I_Z [I_Z R_Z + V_Z] = 12.5 [12.5 \times 0.1 + 5] = 78.125mW$



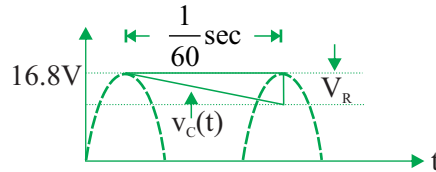Q9. $v_C(t) = (17.8 - 1)e^{-t/RC}$

$\dot{v}_C(t) = \frac{-16.8}{RC} e^{-t/RC}$

$\dot{v}_C(0) = \frac{-16.8}{RC} = \frac{-V_R}{1/60}$



Peak to peak ripple voltage, $V_R = \frac{16.8}{60RC} = \frac{16.8}{60 \times 15 \times 25000 \times 10^{-6}} = 0.75V$

dc output voltage, $V_0 = 16.8 - \frac{1}{2} \times 0.75 = 16.4V$

Q10. Until some value of V_i , both diodes D_1 and D_2 are on. Obviously $I_2 = (I_1 - I) > 0$ and $V_0 = 4.4V$

$I < I_1 \Rightarrow \frac{10 - 4.4}{9.5k\Omega} < \frac{4.4 - 0.6 - V_i}{0.5k\Omega} \Rightarrow V_i < 3.5V$

Thus, $V_i = 3.5V$


For $V_i > 3.5V$, D_2 turns off

and $\frac{V_0 - 10}{9.5k\Omega} + \frac{V_0 - 0.6 - V_i}{0.5k\Omega} = 0 \Rightarrow V_0 = 0.95V_i + 1.07$

Thus, for $V_i > 3.5V$, V_0 linearly increases as V_i increases until V_i equals $9.4V$. Therefore, $V_2 = 9.4V$

For $V_i > 9.4V$, D_1 also turns off and $V_0 = 10V$

$|V_1 - V_2| = |3.5 - 9.4| = 5.9V$

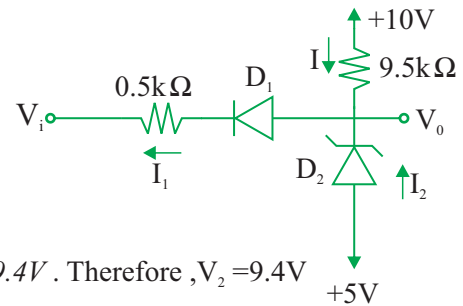


Q11(d). Assume that all three diodes D_1 , D_2 and D_3 are on as it appears so.

Thus, the equivalent circuit gives

$\frac{5 - 0}{5k\Omega} = \frac{0 - 0.7 - (-10)}{5k\Omega} + I_2$

or $I_2 = -0.86mA$ which is not possible.

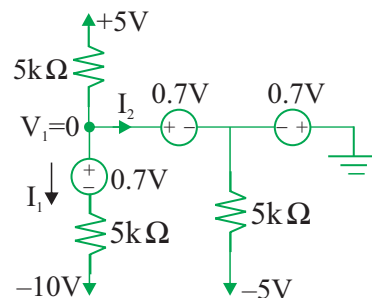Thus, D_2 is off while D_1 and D_3 are on.



Solutions

Test Drill II


The circuit is redrawn below with D_2 off, to examine the state of diodes D_1 and D_2 .

$$I_1 = \frac{5 - 0.7 - (-10)}{5\text{k}\Omega + 5\text{k}\Omega} = 1.43\text{mA}$$

$$I_2 = \frac{0 - 0.7 - (-5)}{5\text{k}\Omega} = 0.86\text{mA}$$

The direction of both currents I_1 and I_2 agree with the direction, the diodes D_1 and D_3 allow the current to flow.

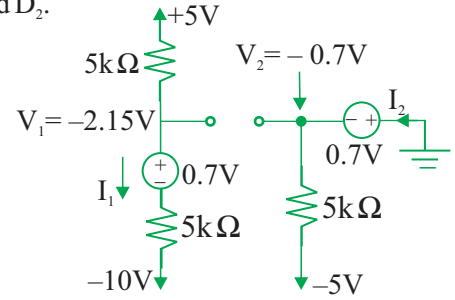The diodes D_1 and D_3 are, in deed, on and $V_1 = 5 - 5 \times 1.43 = -2.15\text{V}$ and $V_2 = -0.7$




Q12(d). The circuit is sketched below for $V_1 = 5\text{V}$ and assuming that both diodes D_1 and D_2 are on.

Note that 1.7V across $1.7\text{k}\Omega$ resistance gives

$$I = 1\text{mA}, V_2 = 5 - 1.7 = 3.3\text{V} \text{ and } I_2 = \frac{3.3 - 0.7}{4\text{k}\Omega} = 0.65\text{mA}$$

Then, $I_1 = I - I_2 = 1 - 0.65 = 0.35\text{mA}$.

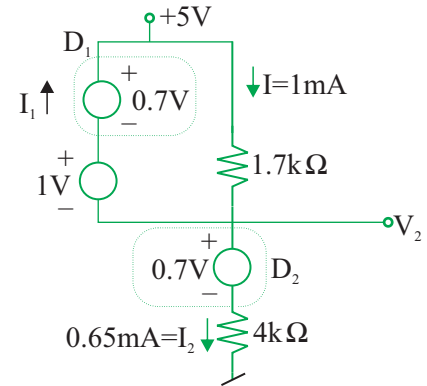But, the direction of I_1 is disallowed by diode D_1 . In fact, D_1 is off.




The circuit with only D_2 on, is again sketched below.

$$\frac{5 - V_2}{1.7\text{k}\Omega} = \frac{V_2 - 0.7}{4\text{k}\Omega} \Rightarrow V_2 = 3.72\text{V}$$

The current through the diode is $\frac{V_2 - 0.7}{4\text{k}\Omega} = 0.75\text{mA}$,

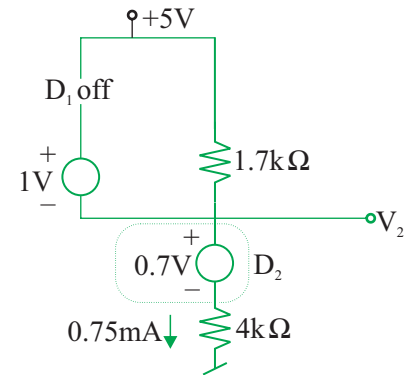the direction of which agrees with the direction in which the diode allows the current to flow.




For $V_2 = 10\text{V}$ assuming diodes D_1 and D_2 on, the circuit is sketched below. Again 1.7V across $1.7\text{k}\Omega$ resistance gives $I = 1\text{mA}$

$$V_2 = 10 - 1.7 = 8.3\text{V} \text{ and } I_2 = \frac{8.3 - 0.7}{4\text{k}\Omega} = 1.9\text{mA}$$

$I_1 = I_2 - I = 1.9 - 1 = 0.9\text{mA}$, the direction of which agrees with the direction, the diode D_1 allows the current to flow.

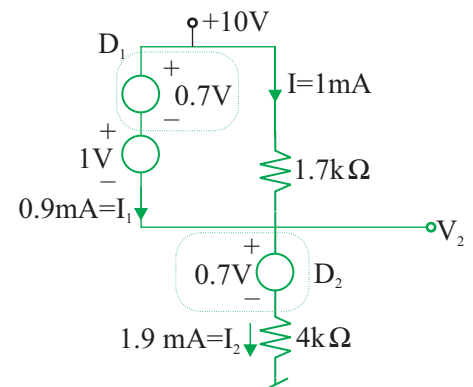Thus, for $V_2 = 10\text{V}$, both diodes D_1 and D_2 are, in deed, on.



Q13(c) On varying V_1 , the node voltage V_2 will remain constant equal to 4.8 V only when the transistor is in saturation and $V_{EC} = 5 - 4.8 = 0.2V$.

$$I_{C,sat} = \frac{V_2}{4k\Omega} = \frac{4.8}{4k\Omega} = 1.2mA \quad \text{and} \quad I_{B,min} = \frac{1.2mA}{80} = 0.015mA$$

$$\text{Base current, } I_B = \frac{5 - 0.8 - V_1}{180k\Omega} A = \frac{4.2 - V_1}{180} mA$$

For the transistor to be in saturation, $I_B \geq I_{Bmin}$, that is, $\frac{4.2 - V_1}{180} \geq 0.015 \Rightarrow V_1 \leq 1.5V$

Thus $V_2 = 4.8V$ for $0 \leq V_1 \leq 1.5V$

Q14. Assume transistor in active mode of operation.

$$\beta = \infty \Rightarrow I_B = 0$$

$$\frac{5 - V_B}{500k\Omega} + \frac{3 - V_B}{500k\Omega} + \frac{-5 - V_B}{44k\Omega} = 0$$

$$\text{gives } V_B = -3.65V \quad \text{and} \quad V_E = -3.65 - 0.65 = -4.3V$$


$$I_E = I_C = \frac{-4.3 - (-5)}{5k\Omega} = 0.14mA$$

$$V_C = 15 - (0.14 \times 50) = 8V$$


$$V_{CE} = V_C - V_E = 8 - (-4.3) = 12.3V$$

$$\text{and power dissipation} = V_{CE} \times I_C = 12.3 \times 0.14 = 1.7mW$$

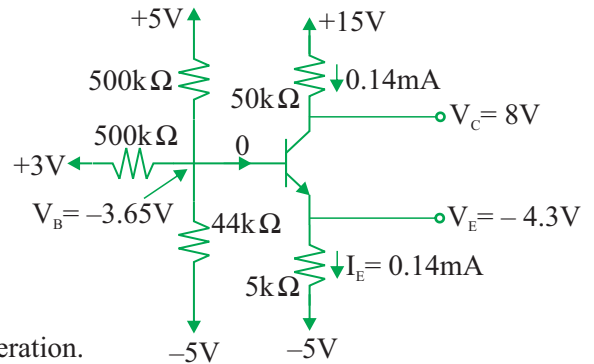Since, $V_{CE} > V_{CE,sat}$, the transistor is, indeed, in active mode of operation.



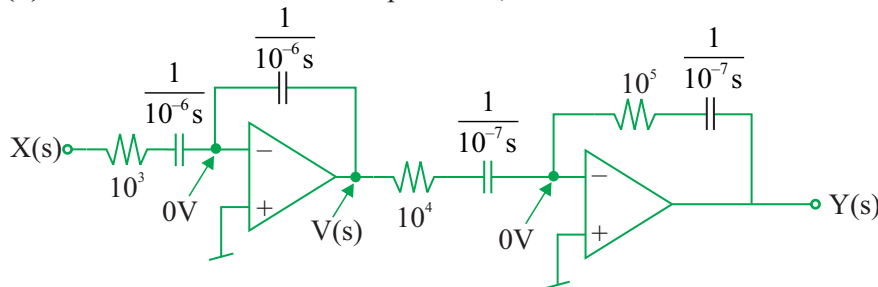Q15 (c). The circuit with transform impedances, is sketched below.





$$\frac{X(s) - 0}{10^3 + \frac{1}{10^{-6}s}} = \frac{0 - V(s)}{\frac{1}{10^{-6}s}} \Rightarrow V(s) = \frac{-X(s)}{10^{-3}s + 1}$$

$$\frac{V(s) - 0}{10^4 + \frac{1}{10^{-7}s}} = \frac{0 - Y(s)}{10^5 + \frac{1}{10^{-7}s}} \Rightarrow V(s) = \frac{-Y(s)(10^{-3}s + 1)}{10^{-2}s + 1}$$

$$\text{Now, } \frac{-X(s)}{10^{-3}s + 1} = \frac{-Y(s)(10^{-3}s + 1)}{(10^{-2}s + 1)} \Rightarrow H(s) = \frac{Y(s)}{X(s)} = \frac{10^{-2}s + 1}{(10^{-3}s + 1)^2} = \frac{s + 10^2}{(s + 10^3)^2}$$


$$\text{and } H(j\omega) = \frac{10^{-2}(j\omega) + 1}{[10^{-3}(j\omega) + 1]^2}$$

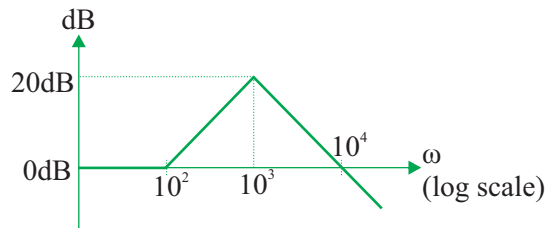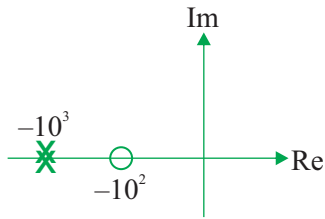The Bode dB plot and pole-zero plot, both are depicted below.



It is obvious that the component of frequency 10^3 rad/sec, is the most amplified with the gain of 20dB in the output. The components of 100 rad/sec and 10^4 rad/sec, are treated with 0dB (unity) gain.

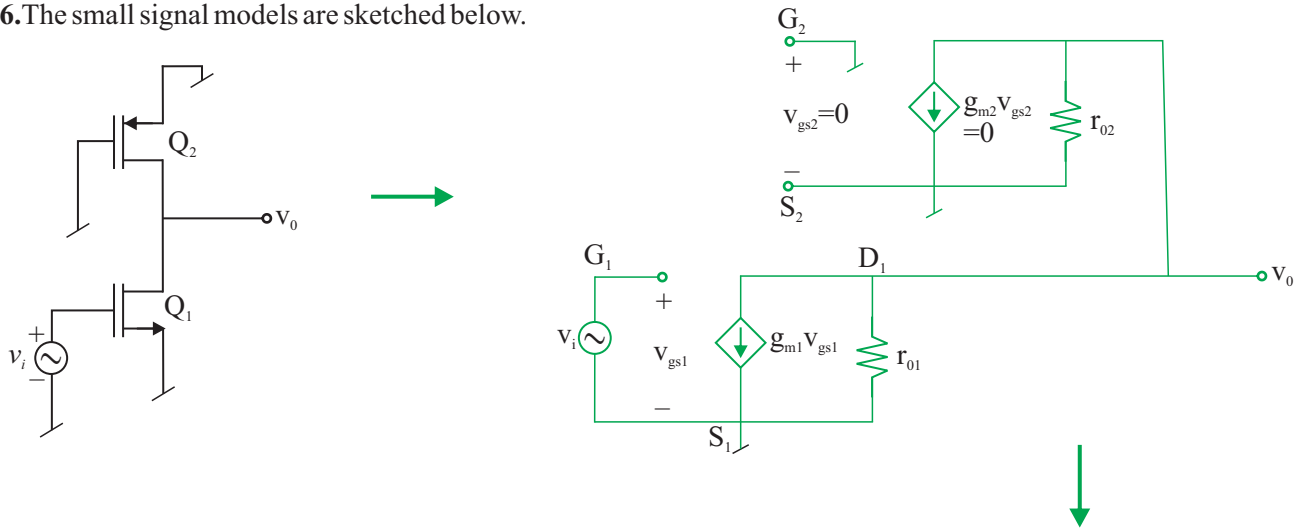Q16. The small signal models are sketched below.



$$v_o = -g_{m1} v_i (r_{01} \parallel r_{02})$$

$$\left| \frac{v_o}{v_i} \right| = g_{m1} (r_{01} \parallel r_{02})$$


$$g_{m1} = \frac{\partial I_{D1}}{\partial V_{GS1}} = \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_{tn}) = 2 \times 10^{-3} (4 - 2) = 4 \text{ mA/V}$$

$$r_{01} = (\lambda_1 I_{D1})^{-1} \text{ where } I_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_{tn})^2 = \frac{1}{2} \times 2 \times 10^{-3} (4 - 2)^2 = 4 \text{ mA}$$

$$r_{01} = (0.01 \times 4 \text{ mA})^{-1} = 25 \text{ k}\Omega$$

$$r_{02} = (\lambda_2 I_{D2})^{-1} = (\lambda_2 I_{D1})^{-1} = (0.025 \times 4 \text{ mA})^{-1} = 10 \text{ k}\Omega$$

$$\left| \frac{v_o}{v_i} \right| = 4 \times 10^{-3} \times \frac{25 \times 10}{25 \times 10} \times 10^3 = 28.6$$

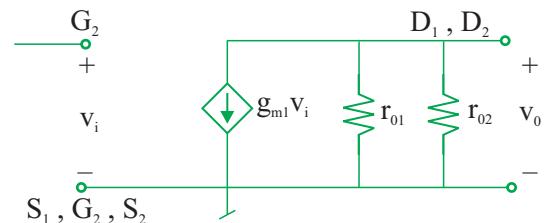

Q17(b). Assume Q1 in saturation mode.

$$I_{D1} = \frac{1}{2} \mu_c C_{ox} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_{t1})^2 ; V_{GS1} = 5V$$

$$= \frac{1}{2} \times 3.2 \times 10^{-3} (5 - 3)^2 = 6.4 \text{ mA}$$

$$I_{D2} = I_{D1} = \frac{1}{2} \mu_c C_{ox} \left(\frac{W}{L} \right)_2 (V_{GS2} - V_{t2})^2$$

$$6.4 \times 10^{-3} = \frac{1}{2} \times 0.4 \times 10^{-3} (V_{GS2} - 3)^2$$


$$(V_{GS2} - 3) = \pm 5.66 \Rightarrow V_{GS2} = 8.66V \text{ or } -2.66V$$

V_{GS2} can not be $-2.66V$. Thus, $V_{GS2} = 8.66V$



$$V_{GS2} = 15 - V_{OUT} \Rightarrow V_{OUT} = 6.34V = \lambda$$

$V_{GD1} = 0 - V_{OUT} = -6.34V < V_{t1}$ and therefore, Q_1 is, in deed, in saturation.

dc model

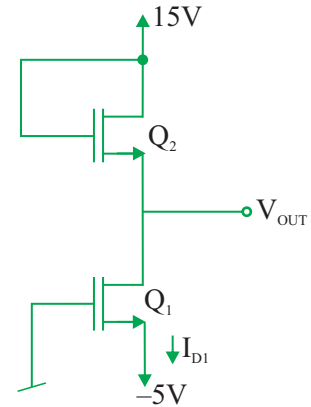

ac model

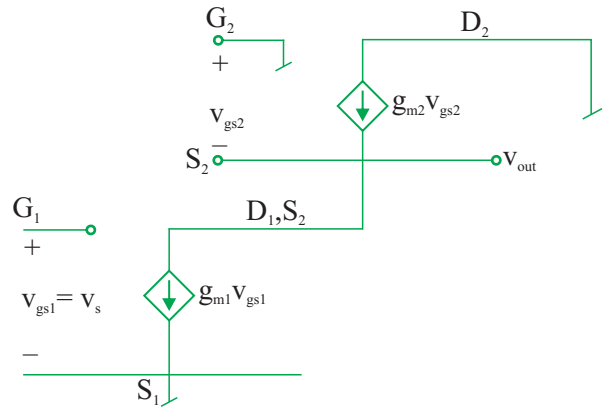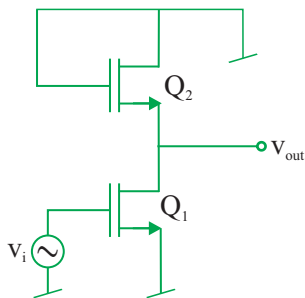

$$\frac{v_0}{v_s} = -\frac{v_{gs2}}{v_{gs1}} = -\frac{g_{m1}}{g_{m2}} ; i_{d1} = i_{d2} \Rightarrow g_{m1} v_{gs1} = g_{m2} v_{gs2} \text{ under no load condn.}$$

$$I_{D1} = \frac{1}{2} \mu_c C_{ox} \left(\frac{W}{L} \right)_1 (V_{GS} - V_{t1})^2 \text{ and } g_{m1} = \frac{\partial I_{D1}}{\partial V_{GS1}} = \mu_c C_{ox} \left(\frac{W}{L} \right)_1 (V_{GS} - V_{t1}) = \sqrt{2I_{D1} \mu_c C_{ox} \left(\frac{W}{L} \right)_1}$$

$$\text{Similarly, } g_{m2} = \sqrt{2I_{D2} \mu_c C_{ox} \left(\frac{W}{L} \right)_2}$$

$$\frac{v_0}{v_s} = -\frac{\sqrt{2I_{D1} \mu_c C_{ox} \left(\frac{W}{L} \right)_1}}{\sqrt{2I_{D2} \mu_c C_{ox} \left(\frac{W}{L} \right)_2}} = -\sqrt{\left(\frac{3.2}{0.4} \right)} = -2.8$$

$$v_0 = -2.8 \times 0.5 \sin \omega t = -1.4 \sin \omega t \Rightarrow \mu = -1.4$$

Thus, $\lambda = 6.34$ and $\mu = -1.4$

Solutions

Test Drill II




Q18(a).

$$I_{BQ} = \frac{5 - 0.7}{(180 + 1) \times 10k\Omega + 2.5k\Omega} = 2.37\mu A$$

$$I_{CQ} = \beta I_{BQ} = 180 \times 2.37\mu A = 0.427mA$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.427mA}{25mV} = 0.017A/V$$
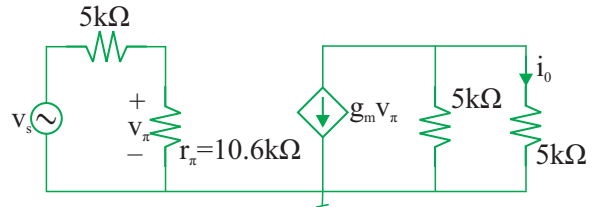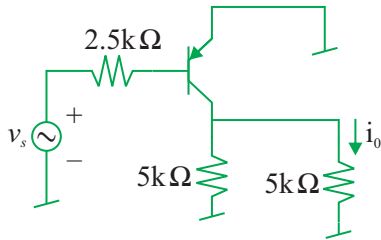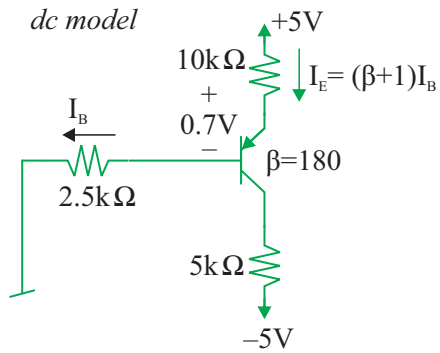
$$r_\pi = \frac{\beta}{g_m} = \frac{180}{0.017} = 10.6k\Omega$$



$$i_o = -\frac{1}{2} g_m v_\pi = -0.5 \times 0.017 \times \frac{10.6}{10.6 + 2.5} v_s = -6.88 \times 10^{-3} v_s$$

$$i_o = -6.88 \times 10^{-3} \times (4 \sin \omega t) \times 10^{-3} A = -27.52 \sin \omega t \mu A$$

$$\lambda = -27.52$$

Q19(b). $\frac{V_x(s) - V(s)}{1k\Omega} = \frac{V(s) - V_Y(s)}{1k\Omega}$

$$V(s) = 0.5V_X(s) + 0.5V_Y(s)$$

$$\text{and } \frac{V_X(s) - V(s)}{R} = \frac{V(s) - 0}{1/Cs}$$

$$V_X(s) = V(s) (1 + sRC)$$

$$V_X(s) = [0.5V_X(s) + 0.5V_Y(s)] (1 + sRC)$$


$$V_X(s) [1 - 0.5 - 0.5sRC] = 0.5(1 + sRC) V_Y(s)$$

$$\frac{V_Y(s)}{V_X(s)} = H(s) = \frac{1 - sRC}{1 + sRC} \text{ and } H(j\omega) = \frac{1 - j\omega RC}{1 + j\omega RC}$$

$$|H(j\omega)| = 1 \text{ and } \angle H(j\omega) = -2 \tan^{-1} \omega RC$$

$$-2 \tan^{-1} \omega RC = -\frac{\pi}{6} \Rightarrow 10^4 \times R \times 10 \times 10^{-9} = \tan\left(\frac{\pi}{12}\right) \Rightarrow R = 2.68k\Omega$$

$$|H(j\omega)| = -1 \text{ regardless of } \omega \text{ and therefore } \lambda = 0.1$$

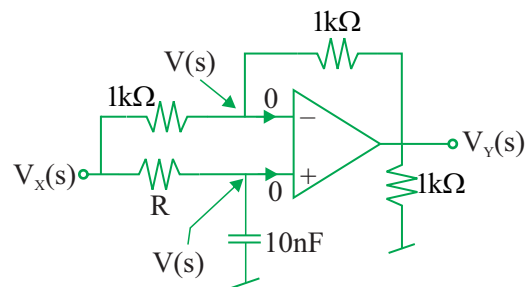

Q20.

$$g_m = \frac{I_C}{V_T} = \frac{1\text{mA}}{25\text{mV}} = 0.4\text{A/V}, \alpha = 1 \Rightarrow r_\pi = \infty \text{ and } V_A = \infty \Rightarrow r_o = \infty$$

SW closed implies $R = 0$ and $v_o = -g_m v_\pi R_L$


KVL around input loop gives

$$v_s - v_\pi - g_m v_\pi \times \frac{1}{j\omega C} = 0$$

$$v_\pi = \frac{v_s \times j\omega C}{g_m + j\omega C}$$

$$v_o = (-g_m R_L) v_\pi \left[\frac{j\omega C}{g_m + j\omega C} \right]$$

$$\frac{v_o}{v_s} = \frac{-g_m R_L}{1 - j \frac{g_m}{\omega C}} \Rightarrow \omega_L = \frac{g_m}{C} \text{ on comparing with general form of gain } |A_v| = \left| \frac{v_o}{v_s} \right| = \frac{A_0}{1 - j \frac{\omega_L}{\omega}}$$

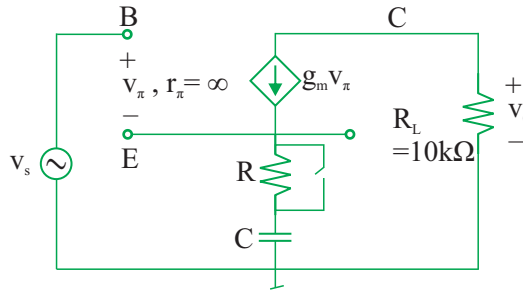

With SW open, again $v_o = -g_m v_\pi R_L$ and $v_s - v_\pi - g_m v_\pi \left(R + \frac{1}{j\omega C} \right) = 0$

$$v_\pi = \frac{v_s \times j\omega C}{g_m + j\omega C(1 + g_m R)} \text{ and } v_o = -g_m R_L v_\pi \left[\frac{j\omega C}{g_m + j\omega C(1 + g_m R)} \right]$$

$$\left| \frac{v_o}{v_s} \right| = \frac{g_m R_L}{(1 + g_m R) + \frac{g_m}{j\omega C}} = \frac{\frac{g_m R_L}{1 + g_m R}}{1 - \frac{j}{\omega} \times \left[\frac{g_m}{(1 + g_m R)C} \right]} \Rightarrow \omega_L^* = \frac{g_m}{(1 + g_m R)C}$$

$$\omega_L^* = 0.2\omega_L \Rightarrow \frac{g_m}{(1 + g_m R)C} = 0.2 \frac{g_m}{C} \Rightarrow 1 + g_m R = 5 \text{ and } R = \frac{4}{g_m} = \frac{4}{0.04} = 100\Omega$$

Q21(c). Fig.(1) ; Let the input signal to block with gain $A_1 = 10^3$ be v_E .

$$v_o^* = A_1 A_1 v_E + A_2 v_{ni}, \quad v_E = v_i - \beta v_o^*$$

$$v_o^* = A_1 A_2 v_i - A_1 A_2 \beta v_o^* + A_2 v_{ni}$$

$$v_o^* = \frac{A_1 A_2}{1 + A_1 A_2 \beta} v_i + \frac{A_2}{1 + A_1 A_2 \beta} v_{ni} = \frac{10^4}{1 + 10^2} v_i + \frac{10}{1 + 10^2} v_{ni} \cong 100 v_i + 0.1 v_{ni}$$

$$(\text{SNR})_o = \frac{100}{0.1} \times \frac{v_i}{v_{ni}} = 1000 (\text{SNR})_i$$

$$\text{Fig.(2); } v_o^* = A_1 A_2 v_E = A_1 A_2 [v_i + v_{ni} - \beta v_o^*]$$

$$v_o^* = \frac{A_1 A_2}{1 + A_1 A_2 \beta} v_i + \frac{A_1 A_2}{1 + A_1 A_2 \beta} v_{ni} = \frac{10^4}{1 + 10^4 \times 0.01} v_i + \frac{10^4}{1 + 10^4 \times 0.01} v_{ni} \cong 100 v_i + 100 v_{ni}$$

$$(\text{SNR})_o = \frac{100}{100} \times \frac{v_i}{v_{ni}} = (\text{SNR})_i$$


Amplifier configuration of Fig(1) has better noise immunity.

Q22(d). $T(f) = |T(f)| \angle T(f) = \frac{\lambda}{(1+10^{-10}f^2)^{3/2}} \angle -3 \tan^{-1} 10^{-5} f$

$-3 \tan^{-1} 10^{-5} f = -180^\circ$ gives $f = 10^5 \tan 60^\circ = \sqrt{3} \times 10^5 \text{ Hz}$

$$|T(f)|_{f=\sqrt{3} \times 10^5} = \frac{\lambda}{\left[1+10^{-10} \times (\sqrt{3} \times 10^5)^2\right]^{3/2}} = \frac{\lambda}{8}$$

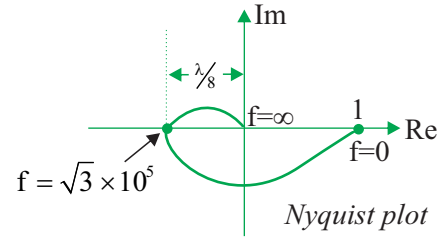For the amplifier to be stable $\frac{\lambda}{8} < 1$ or $\lambda < 8$.



Q23. For $v_0 = 0$, $I_{D3} = 2 \text{ mA} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS3} - V_T)^2$

$$2 \times 10^{-3} = \frac{1}{2} \times 2 \times 10^{-3} (V_{GS3} - 1)^2 \Rightarrow V_{GS3} = -0.414 \text{ V or } 2.414 \text{ V}$$

V_{GS3} must be greater than $V_T = 1 \text{ V}$. Thus, $V_{GS3} = 2.414 \text{ V}$

$V_{G3} = 2.414 \text{ V}$ and current I_{D2} in M_2 is 0.5 mA .

$$R = \frac{12 - V_{G3}}{0.5 \text{ mA}} = \frac{12 - 2.414}{0.5 \text{ mA}} = 19.2 \text{ k}\Omega$$

Note that $V_{GD3} = V_{G3} - V_{D3} = 2.414 - 12 = -9.586 \text{ V} < V_T$.

M_3 is, indeed, in saturation.

Q24(c). $V_0 = V_Z \left[1 + \frac{32 \text{ k}\Omega}{40 \text{ k}\Omega}\right] = 5.6 \times 1.8 \cong 10 \text{ V}$

Set I_F for minimum bias current of 1 mA to get


$$R_F = \frac{10 - 5.6}{1 \text{ mA}} = 4.4 \text{ k}\Omega$$

The maximum Zener current should be no more than 1.25 mA .

Set $I_{D1} = 0.25 \text{ mA}$

$$I_2 = \frac{5.6 + 0.7}{30 \text{ k}\Omega} = 0.21 \text{ mA}$$
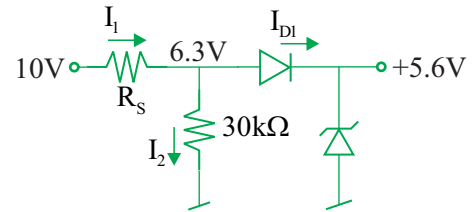
$$I_1 = \frac{10 - 6.3}{R_s} = (0.21 + 0.25) \text{ mA} \Rightarrow R_s \cong 8 \text{ k}\Omega$$



Q25. $I_x = \frac{V_1 - V_2}{R} \Rightarrow \frac{0.25 - (-0.25)}{R} = 5 \text{ mA} \Rightarrow R = 100 \Omega$

$$\frac{V_{01} - V_1}{R_2} = I_x \Rightarrow V_{01} = V_1 + I_x R_2 = 0.25 + 5 \times 10^{-3} \times 1000 = 5.25 \text{ V}$$

$$V_{02} = -0.25 \text{ V and } V_{01} - V_{02} = 5.25 - (-0.25) = 5.5 \text{ V}$$

www.mechasoft.co.in